

# Assignment - 1

## ELECTRONIC DEVICES

Name: Nikhil Chowdary

Roll No. 160120735157

Sec: ECE-3

Semister: III<sup>rd</sup> sem

- ① A Si diode operating at room temp. with a forward voltage of 650mV has a reverse saturation current of 20nA. Determine its Dynamic resistance.

Given  $I_{Ss} = 20\text{nA}$ ,  $V_f = 650\text{mV}$ ,  $V_T = 20\text{mV}$ ,  $\eta = 2$  ( $\because$  Si diode)

we know that Dynamic resistance ( $r$ ) =  $\frac{\eta V_T}{I_0 \cdot e^{V/\eta V_T}}$

$$r = \frac{2 \times 26 \times 10^{-3}}{20 \times 10^{-9} \cdot e^{\frac{650}{2 \times 26}}} = \frac{52 \times 10^{-3}}{20 \times 10^{-9} \times 268337.287} \Omega$$

$$r = \frac{52}{5.366} = 9689 \Omega$$

- ② A diode has a leakage current of 10mA at a certain Temp. Assess its value when the temperature is increased by 25°C.

we know that  $I_2 = I_1 \times 2^{\frac{T_2 - T_1}{10}}$

given  $I_1 = 10\text{mA}$ .

$$\Rightarrow I_2 = 10\text{mA} \times 2^{2.5}$$

$$I_2 = 56.5\text{mA}$$

③ A Si diode indicates forward current of 2mA and 10mA when diode voltage are 0.6V and 0.7V resp. Estimate the operating temp. of the diode junction.

Given  $I_{0.6} = 2\text{mA}$  ,  $V_D = 0.6$

$\eta = 1$  ( $\because$  Si diode)

$I_{0.6} = 10\text{mA}$  ,  $V_D = 0.7$

we know that

$$I = I_{sh} e^{\frac{-V_D}{\eta V_T}}$$

$$2 = I_{sh} \cdot e^{\frac{0.6}{2V_T}} \quad \text{--- (1)}$$

$$\text{also } \Rightarrow 10 = I_{sh} \cdot e^{\frac{0.7}{2V_T}} \quad \text{--- (2)}$$

$$\frac{(2)}{(1)} \Rightarrow 5 = e^{\left(\frac{0.7}{2V_T} - \frac{0.6}{2V_T}\right)}$$

$$\Rightarrow 5 = e^{\frac{1}{V_T} (0.05)}$$

$$\ln(5) = \frac{1}{V_T} (0.05) \Rightarrow V_T = \frac{0.05}{\ln 5}$$

$$V_T = 0.0310$$


$$V_T = \frac{T}{11,600} = 0.310$$

$$T = (11,600 \times 0.310) \text{K}$$

$$T = 360.374 \text{K}$$

$$T = 87.37^\circ\text{C}$$

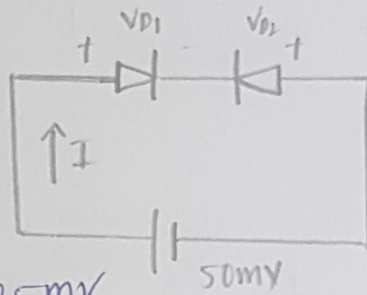④ The circuit given below consists of two identical diodes with  $\eta = 1$ . Assume  $V_T = 25 \text{ mV}$ . Evaluate  $V_{D1}$  and  $V_{D2}$ .



Given  $\eta = 1, V_T = 25 \text{ mV}$

And from circuit  $V_{D1} + V_{D2} = 50 \text{ mV}$

We know that  $I = I_{sh} (e^{V_D / \eta V_T} - 1)$

$$\cancel{I_{sh}} \left[ e^{\frac{V_{D1}}{V_T}} - 1 \right] = -\cancel{I_{sh}} \left[ e^{\frac{-V_{D2}}{\eta V_T}} - 1 \right]$$

$$e^{\frac{V_{D1}}{25}} + e^{\frac{-V_{D2}}{25}} = 2.$$

$$e^{\frac{V_{D1}}{25}} + e^{-\left(\frac{0.05 - V_{D1}}{V_T}\right)} = 2.$$

$$e^{V_{D1}/25} \left[ 1 + e^{-0.05/25} \right] = 2.$$

$$\frac{V_1}{25} = \ln 2 \Rightarrow V_1 = 0.693 \times 25 \text{ mV} \Rightarrow V_1 = 0.01732 \text{ V}$$

as  $V_1 + V_2 = 0.05 \text{ mV}$


$$V_2 = 0.05 - 0.01732$$

$$V_2 = 0.033 \Rightarrow V_1 = 0.017 = 17.32 \text{ mV}$$

$$V_2 = 33 \text{ mV}$$



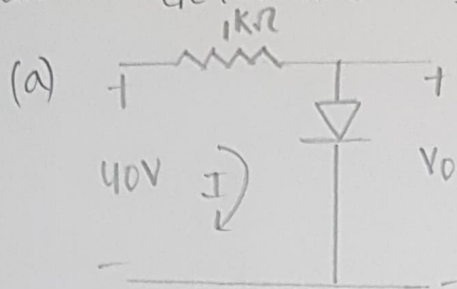- (5) Interpret the following circuits assuming ideal diodes and determine  $I$  and  $V_0$ .




As diode is in Forward bias and Ideal. It can be considered as shortcircuit. By applying KVL we have.

$$-40 + 1000I = 0.$$

$$\Rightarrow I = \frac{40}{1000} = 4\text{mA}.$$
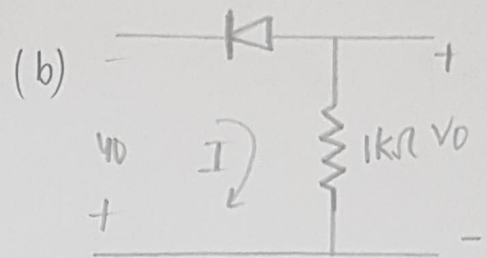
$$\Rightarrow V_0 = IR = \frac{40}{1000} \times 0 = 0\text{V}$$



As diode is in Forward bias and Ideal it can be replaced by a short circuit and.



$$I = \frac{-V}{R} = \frac{-40}{1000}$$

$$P = -40\text{mA}$$

$$V_0 = IR = -40 \times 10^{-3} \times 10^3$$

$$\boxed{V_0 = -40\text{V}}$$

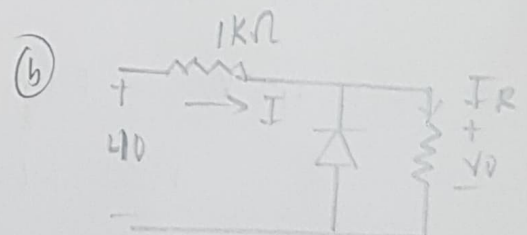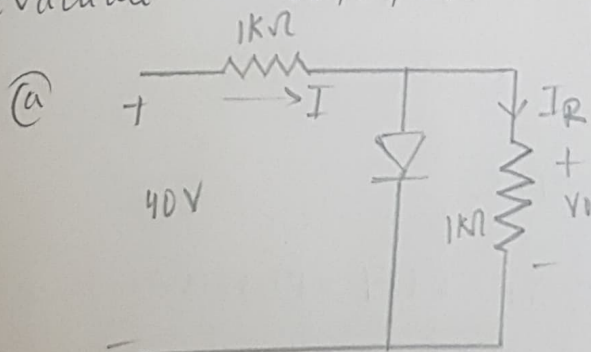- (6) Evaluate  $V_0$ ,  $I$ ,  $P_R$  and  $I_0$  assuming ideal diodes.



(a) As the diode is connected in forward bias - we can replace it by short circuit then no current passes through.

$$1k\Omega \text{ i.e., } \boxed{I_R = 0}$$

$$I = \frac{V}{1k\Omega} = \frac{40}{1k\Omega} = 40mA$$

$$I_R = 0 \Rightarrow V = I_R \times 1k\Omega = 0$$




(b) As the diode is connected in reverse bias it can be replaced by open circuit. i.e.,  $\boxed{I_D = 0}$  and

$$I = I_R = \frac{V}{R_{eff}} = \frac{V}{2k\Omega} = \frac{40}{2k\Omega} = 20mA$$

$$\Rightarrow I = I_R = 20mA, \quad I_D = 0$$

$$V_0 = I_R \times 1k\Omega = 20mA \times 1k\Omega = 20V$$

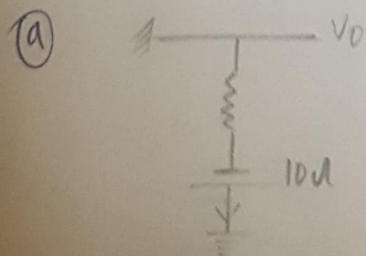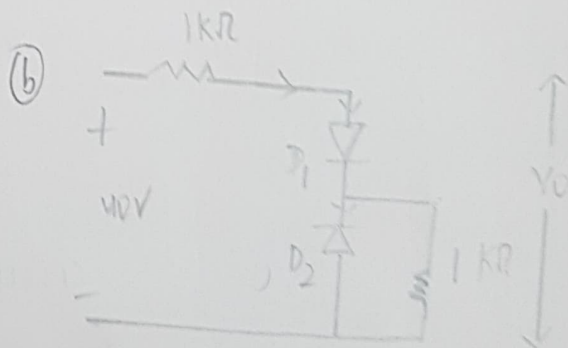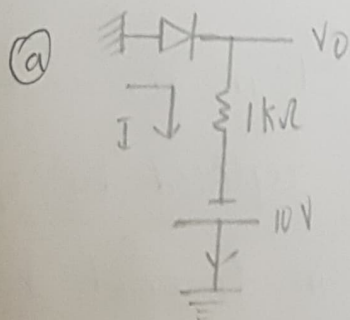
7 Find  $I$  and  $V_0$  assuming ideal diodes.



As diode is connected in forward bias - It can be replaced by short circuit  $\Rightarrow V_0 = 0$ .

$$I = \frac{V}{R} = \frac{10}{1k\Omega} = 10mA$$

⑥

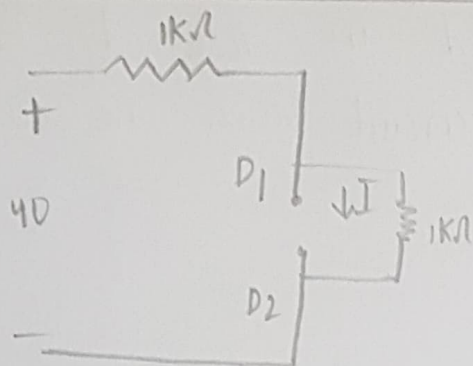

Here  $D_1$  is in Forward bias  
 can replace it by short circuit  
 $D_2$  is in reverse bias  
 can be replaced by open circuit



circuit as shown in fig. since  $I = 0$ .

$$V_0 = \frac{1 \times 40}{1+1} = \frac{40}{2} V = 20V.$$

$$I = 0, V_0 = 20V.$$

⑧

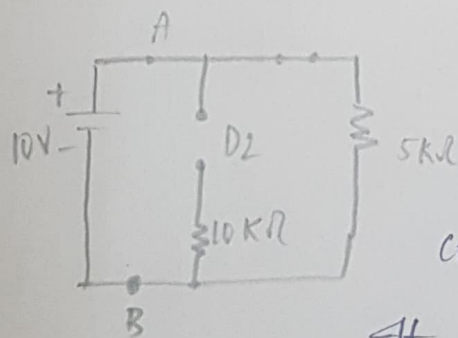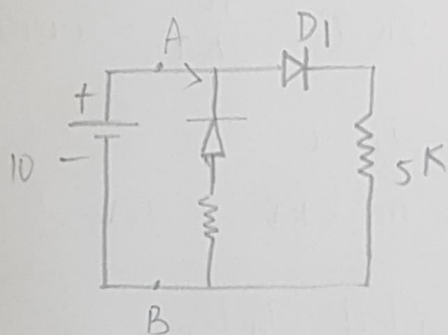Determine the impedance between points A and B assuming ideal diodes.



Since  $D_2$  is in reverse bias  
 it can be replaced by open circuit.  
 $D_1$  is in forward bias  
 it can be replaced by short circuit.




$$Z = R = 5k\Omega \quad [Z = 5k\Omega]$$

$$[Z = 5k + 0j]$$

Ans



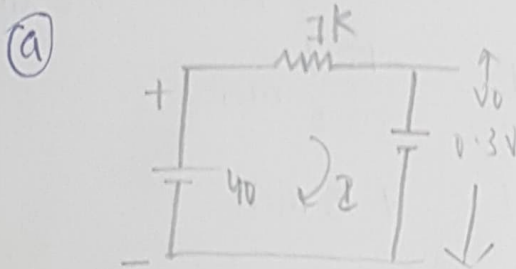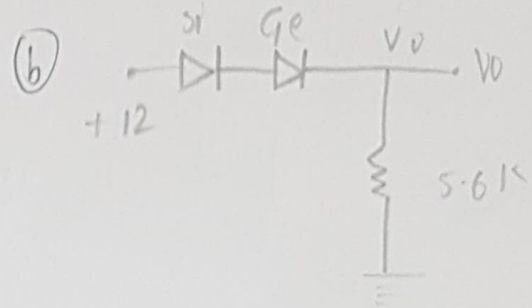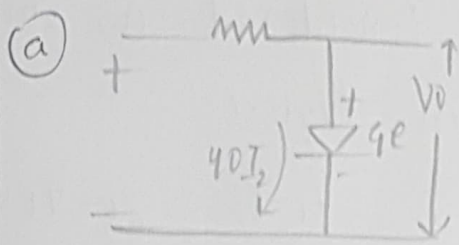9. Analyse the circuit given below assuming practical diodes and estimate  $I$  and  $V_0$ .




Since Ge diode is practical it can be replaced by voltage source of  $0.3V$

Applying KVL

$$-40 + I \times 1000 + 0.3 = 0$$

$$\Rightarrow I = \frac{39.7}{1000} = 39.7 \text{ mA}$$

$$V_0 = 0.3$$

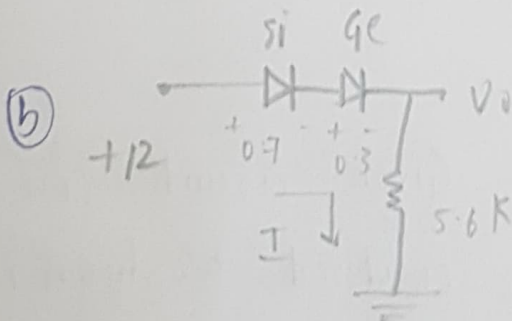


Here Si diode can be considered as voltage source of  $0.7V$  and Ge diode can be

considered as voltage source of  $0.3V$  as shown in figure.

$$\Rightarrow V_0 = 12 - 0.7 - 0.3 = 11V \Rightarrow I = \frac{V_0}{5.6} = 1.96 \text{ mA}$$

10. Assess the value of  $I$  in the following circuit given

$$V_{Si} = 0.7V$$

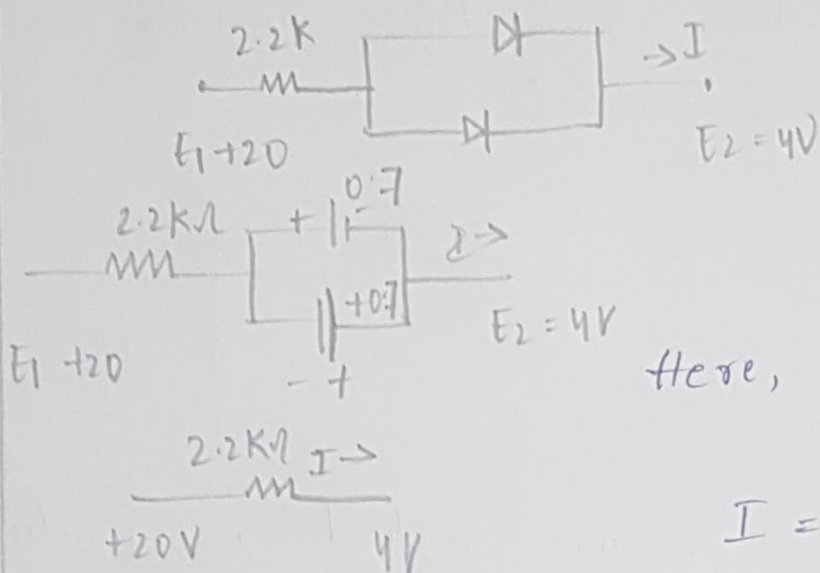


Given circuit can be considered as shown in figure.

$$\text{Here, } I = \frac{E_1 - E_2}{R} = \frac{20 - 4.03}{2.2 \times 1000} \text{ A}$$

$$I = \frac{15.7}{2.2} \text{ mA}$$

$$I = 7.13 \text{ mA}$$

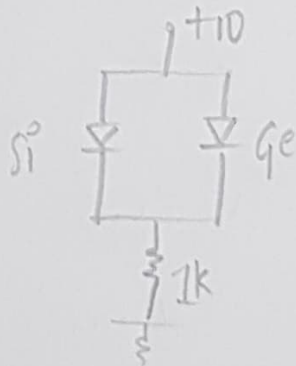11) Analyze the circuit below and determine  $V_0$  given  $V_r = 0.7 \text{ V}$  for Si and  $0.2 \text{ V}$  for Ge.





Given circuit can be considered as shown in figure.

$$-10 + 0.3 + 1000 I = 0$$

$$\Rightarrow I = 9.7 \text{ mA}$$


$$V_0 = IR = 9.7 \text{ mA} \times 1000 \Omega$$

$$\boxed{V_0 = 9.7 \text{ V}}$$

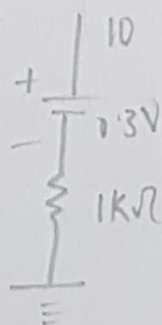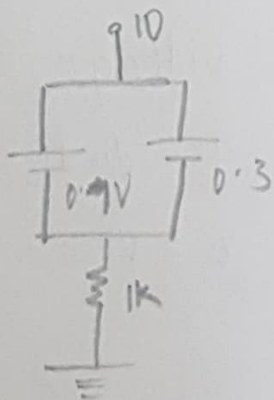




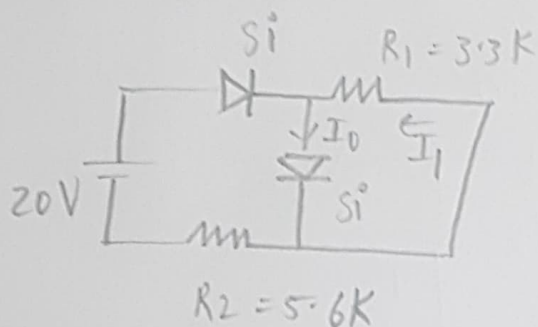- (12) Determine  $I_0$  in the circuit below considering practical diode.



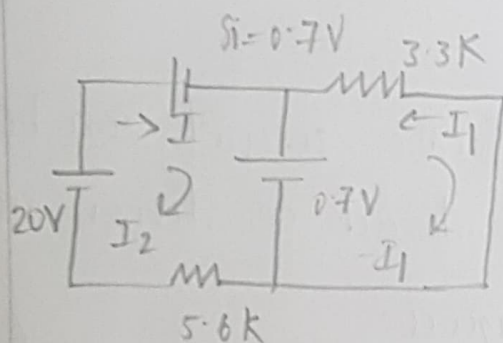Given circuit can be considered as circuit shown in figure. Applying KVL in loop 1.



$$-20 + 0.7 + 0.7 + I_2 (5.6K) = 0$$

$$I_2 = \frac{20 - 0.7 - 0.7}{5.6 \times 1000} = \frac{18.6}{5.6 \times 1000}$$

$$I_2 = 3.32 \text{ mA}$$

Applying KVL in loop 2.

$$-0.7 - 3.3K I_1 = 0 \Rightarrow I_1 = \frac{-0.7}{3.3 \times 1000} = -0.212 \text{ mA}$$

Here Applying KCL at node A.

$$\text{we have, } I_2 + I_0 = -I_1$$

$$I_0 = I_1 + I_2 = 3.32 - 0.212$$

$$I_0 = 3.11 \text{ mA}$$

$$\therefore I_1 = 0.21 \text{ mA}, I_2 = 3.32 \text{ mA}, I_0 = 3.11 \text{ mA}$$

(B) Assess the value of  $V_{D1}$ ,  $V_{D2}$ ,  $I$  and  $I_R$  assuming practical diodes.


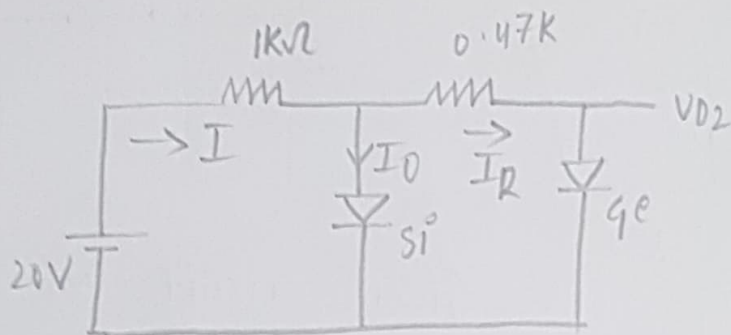


Fig.

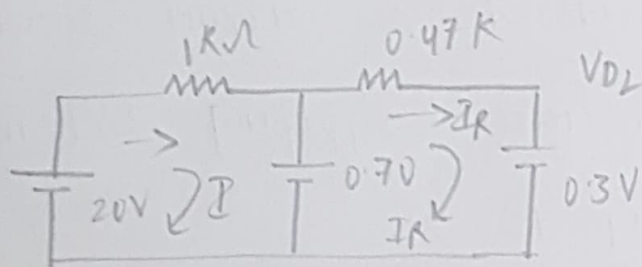

Given circuit can be considered as shown in figure.

$$I_0 = I - I_R \quad (\text{Node equation})$$

Applying KVL for first loop.

$$-20 + 1000I + 0.7 = 0$$

$$\Rightarrow I = \frac{19.3}{1000} = 19.3 \text{ mA}$$

Applying KVL for second loop.

$$-0.7 + 470 I_R + 0.3 = 0$$

$$470 I_R = 0.4 \Rightarrow I_R = 0.85 \text{ mA}$$

$$I_0 = 19.3 - 0.85 = 18.44 \text{ mA}$$


$\therefore$  Applying KVL for loop 2

$$\text{we have } -0.7 + 0.47k I_R + V_{D2} = 0$$


$$V_{D2} = 0.39 \text{ V}$$

$$V_{D2} = 0.39 \text{ V}, I = 19.3 \text{ A}, I_R = 0.85 \text{ mA}, I_0 = 18.44 \text{ mA}$$

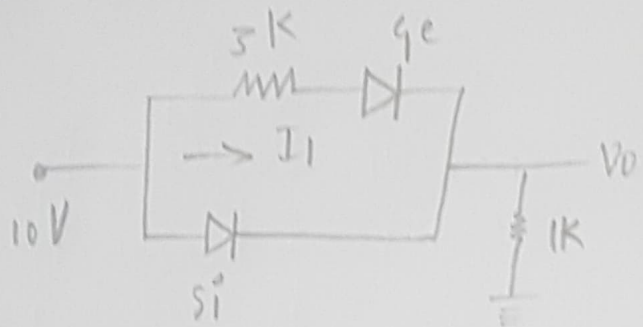(14) Estimate  $V_0$  and  $I_1$  in the circuit below assuming practical diode.



Sol:

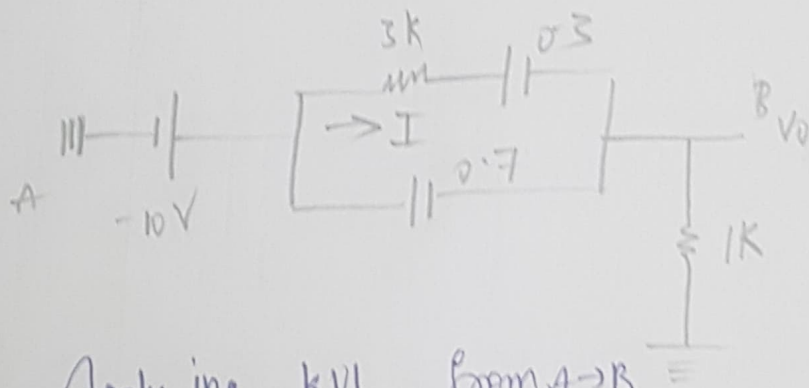

Applying KVL from A  $\rightarrow$  B

we have  $-10 + 0.3 + V_0 = 0$

$$V_0 = 9.7V$$

Applying KVL in loop

$$3000I + 0.3 - 0.7 = 0$$

$$I = \frac{0.4}{3000} = 0.13 \text{ mA}$$

$$V_0 = 9.7 \Rightarrow I = 0.13 \text{ mA}$$